

Ham 37 – CI-V MOD Control & Audio Hub

Dr. Marc & Rosemary © 220511

1. The CI-V manual or data (MOD) control & audio hub is for radios without a sound card and data ports.

- Remote computer operation of a ham radio is often highly desirable.
- This is the simplest, passive design compiled from myriad sources.
- Commercial interfaces are available, but they tend to be expensive bloatware.
- Homebrew solutions are across the web. Many are based on poor information.
- The objective is to avoid opening the radio or modifying any circuit boards.

2. The radio is really just a computer with RF in/out, audio in/out, and control in/out.

- Control is digital via USB to RS232 serial cable operating at 3.3 V levels.
- Audio is analog via speaker-out and mic-in.
- The computer and the radio audio inputs are for electret mics.
- So, the connector has about 5 - 8 Vdc voltage applied.
- A small radial disk capacitor must isolate the DC from the hub.
- The capacitor must be large enough to not filter voice bass. (~1µFd).

3. Fortunately, since 1990, many rigs have a common interface called CI-V.

- The interface allows normal programming of memory by software like Chirp.
- The same cable and connector can provide control, including PTT.
- Icom developed CI-V but many other manufacturers adopted parts of it.

4. The diagram shows a connection hub between the computer and radio.

- The diagram shows all jacks with capacitors and resistor matching network.
- Jacks are 3.5mm, but (1) 2.5mm with (1) RJ45 & (1) RJ14 to radio mics.
- For 'K-head' connector, space 12 mm center from the 2.5mm {8} to 3.5mm. {6}
- The top pin represents the ring, the middle is sleeve, the bottom is tip.

5. The CI-V from Icom is a stereo, 3-conductor, 3.5 mm plug. {4}

- The hub splits the digital-control and the audio-out.

6. CI-V control is the same stereo, 3-conductor, 3.5 mm jack. {5}

- Connect to an USB adapter with FTDI FT232RL chip.
- This is the same cable used for programming memory.



7. Connect radio speaker-out through a network to computer audio-in. {3}

8. Connect the computer audio-output {1} through a network to the radio-mic.

- For Icom, a jumper must connect from mic Earth [E] to PTT [P].
- When P line = 0, then PTT is active low and mic is grounded.
- The connector varies with rigs, but can easily be adapted from the RJ-45/14.

9. The computer audio may derive from a USB to audio adapter if needed.

10. If PTT is not available from CI-V, connect the I/O pin from Raspi. {7}

- A current limiting resistor of 330 Ω protects the computer from shorting.
- A controlled USB 232 can use TxD or Rst depending on software.

11. Several pads for soldering jumper wires are available along the board edge.

- JP2: V=Vdc, C=[], T=Txd, P=PTT, E=Mic e, G=gnnd.
- JP1: P=PTT to E= Mic e by RJ45 to mic on radio.

$$105 = 10 \text{ pF} * 10^5$$

$$105 = 1 \text{ } \mu\text{F}$$

12. Few parts are needed besides connectors.

- Capacitors: radial, ceramic disk: (2) 1 µFd, 15 Vdc.
- Resistors: 1/8-watt axial: (2) 10 Ω, (2) 787 Ω, (2) 330 Ω.
- R1tip= R3tip= 787, R1gnnd= R3gnnd= 10, R7tip = R7ring= 330 Ω.


13. Radio options are Icom on 2 & 4, Yaesu on 9 & 4, Baofeng 'K-head' on 6 & 8.

14. Appropriate software is necessary to control the PTT, and to route the audio in the computer through the serial ports. A test configuration is on the next page.

15. This info reasonably configures radios to connect with EchoLink, AllStar, or a stand-alone control.

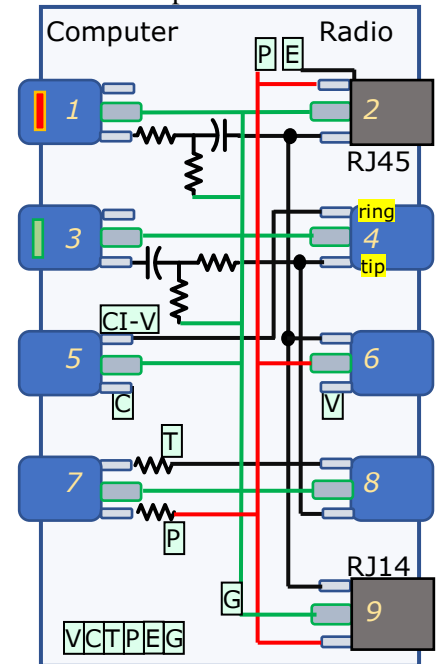16. Create a circuit board for the connectors.

- Use larger spacing so less experienced users can solder the components.
- Make fit perhaps Raspberry Pi size or slimmer: 82mm x 56mm.



Bottom of board is ground plane.

#	Connector	To
1	3 pin stereo 3.5mm	Comp spkr
2	RJ 45	Icom mic
3	3 pin stereo 3.5mm	Comp mic
4	3 pin stereo 3.5mm	Icom spkr2
5	3 pin stereo 3.5mm	FTDI CI-V
6	3 pin stereo 3.5mm	BF mic
7	3 pin stereo 3.5mm	Raspi PTT
8	3 pin stereo 2.5mm	BF spkr
9	RJ 14	Yaesu mic

#	Tip	Ring	Sleeve
1	Comp spkr		gnd [G]
2	RJ 45	See box	
3	Comp mic		gnd [G]
4	Ic spkr2	CI-V	gnd [G]
5	[C]	CI-V /FTDI	gnd [G]
6	8Vdc[V] /BF mic+		mic-/PTT/Rx
7	resistor PTT	resistor Txd	gnd [G]
8	spkr+ /BF Txd [T]		gnd [G]
9	RJ 14	See box	

#	Device	Vend
6	3.5 stereo	Kycon STX-3120-3
1	2.5 stereo	Kycon STX-2000-3
1	RJ 45, 8P	Kycon GMX-S-88
1	RJ 14, 6P	Kycon GMX-S-66
2	1 µFd, 15 V	Radial 105

or GDLX, GLX, GSX



RJ-45 Pins	RJ-14 Pins
4: PTT [P]	1: PTT [P]
5: Mic e [E]	2: Mic
6: Mic	3: Gnd [G]
7: Gnd [G]	

