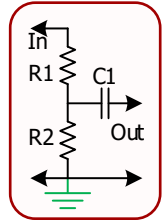


## Ham 38 - Impedance, Attenuation & DC block

Dr. Marc & Rosemary © 220404

1. **Nerd Alert:**

- a. This is a topic that requires several calculations. The most difficult is multiply or divide.
  - b. The design includes all the electrical topics encountered on the Technician exam.
  - c. You passed that, so I know you can do this.
2. Audio has speaker or headphone output and microphone input. But then things get interesting.
    - a. A typical speaker impedance ( $Z$ ) operates at  $8\ \Omega$  (Ohms). Headphone impedance is  $30\text{--}60\ \Omega$ .
    - b. Electret microphones are nominal  $800\ \Omega$ . Other type mics operate with impedance for their purpose.
    - c. Electret has a voltage applied to the mic to energize. Icom applies  $8\ \text{Vdc}$  with current of  $10\ \text{ma}$ .



3. Rules of thumb for connection.

- a. Amateur equipment is voice only with range of  $300\text{--}3000\ \text{Hz}$ .
- b. Music has a range of  $20\text{--}20,000\ \text{Hz}$ .
- c. The mics and speakers for music and voice are not interchangeable with equal performance.
- d. Output  $Z$  of the source must be lower than input  $Z$  of the equipment.
- e. If mic has low  $Z$  and equipment has high  $Z$ , the mic likely will have inadequate energy to drive the input.
- f. Maximum power transfer occurs with the source matches the load.
- g. If using other than electret, place a large disk capacitor in series with the mic input to remove the  $\text{Vdc}$ .
- h. Capacitance must be large enough to pass low frequency voice, ( $\sim 1\ \mu\text{Fd}$ ).
- i. Attenuation and impedance matching is easiest with a voltage divider, which is a 'T' network.

4. If creating a remote-control radio, connect the audio out from the radio to the computer.

- a. The attenuator resistor equals the impedance of the opposite port.....
- b. The sum of  $R_1 + R_2 = Z_{out}$ , so  $R_1 = Z_{out} - R_2$ .....
- c. The resistors create a voltage divider which attenuates  $V_{in}$ .....
- d. The series current depends on the voltage of audio in. ....
- e. By substitution, the output voltage depends on the resistor ratio. ....
- f. Check that the output current is low enough to protect the circuit. ....

$$R_2 = Z_{in}$$

$$R_1 = Z_{out} - Z_{in}$$

$$V_{in} = (R_1 + R_2) I_{in}$$

$$V_{out} = R_2 / (R_1 + R_2) V_{in}$$

$$V_2 = R_2 * I_{out}$$

5. Attenuation in decibels (dB) depends on the ratio of  $V_{in} / V_{out}$ .

- a. The input output voltage ratio depends on the same resistor ratio.....
- b. The decibels are defined. ....

$$V_{in} / V_{out} = (R_1 + R_2) / R_2$$

$$\text{dB} = 20 \log_{10} (V_{in} / V_{out})$$

6. Consider an input from a speaker port ( $8\ \Omega$ ) and an output to an electret port ( $800\ \Omega$ ).

- a. Size resistor  $R_2$ .....
- b. Size resistor  $R_1$ .....
- c. ....
- d. Series current .....
- e. Output voltage.....
- f. Works even for a line voltage of  $1\ \text{V}$ ,  $1\ \text{ma}$ .....

$$R_2 = 8$$

$$R_1 = 800 - 8 = 792$$

$$V_{in} = 792 I_{in}$$

$$V_{out} = 8 / 800 V_{in} = 0.01 V_{in}$$

$$V_2 = 8 * I_{out}$$

Attenuation


- a. Voltage ratio.....
- b. dB.....

$$V_{in} / V_{out} = 800 / 8 = 100$$

$$\text{dB} = 20 \log_{10} (100) = 40$$

7. The diagram shows a connection interchange between the computer and radio.

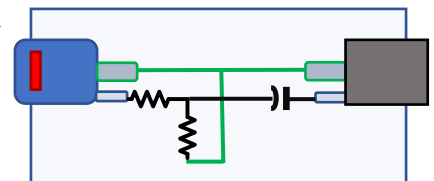- a. Preferably build on a circuit board, but the connections are simple enough to hand wire.



8. Consider constructing for a headphone as source feeding an electret mic input.

- a.  $R_2$  is  $45$ ,  $R_1 = 800 - 45 = 755$ ,  $V_{out} = .056 V_{in}$ ,  $I_{out} = .056/45 = 1\ \text{ma}$ ,  $\text{dB} = 25$ .
- b. To assure a lower impedance is feeding into a higher, use R for headphone.

