

**Ham 70 – License, Power**  
Dr. Marc & Rosemary © 221018

1. The previous articles discussed impedance. Impedance is the ratio of voltage to current.  $Z = V/I$ .
2. Apparent power is the product of voltage and current oscillating at a frequency (AC).
  - a. It is measured in Volt-Amps.  $S = VI^*$ .
  - b. Real power (P) is from a resistor and lies on the x-axis. It is measured in Watts
  - c. Reactive power (Q) is from reactance (inductor & capacitor). It is measured in Volt-Amp-Reactive, (Wattless) Reactive is identified with a 'j' and lies on the vertical axis.
3. The phase angle 'φ' between apparent (S) and real power (P) is identical to the impedance angle.
  - a. Power factor is the ratio of real power to apparent power. It is also the COSINE (Cos) of the phase angle.  
 $pf = P/S = \text{Cos } \phi$ .
  - b. Real power is apparent power times power factor.  $P = S * pf$  or  $P = S * \text{Cos } \phi$   
 $P = VI \text{Cos } \phi$
  - c.  $\text{Cos } 30 = 0.866$        $\text{Cos } 45 = 0.707$        $\text{Cos } 60 = 0.5$
4. Real power depends only on the current and resistance.  
From impedance:  $V = IR$   
From power:  $S = VI^*$   
Combine:  $S = I^2 R$ , but only resistor so  $P = I^2 R$
5. Ideal capacitors and inductors have no resistance.  
An inductor and capacitor oscillate at a resonant frequency.
6. Life is good. Enjoy!

