


Ham 46F – ASL Radio: Cables Made Simple

Dr. Marc & Rosemary © 230126

1. One of the secrets of a successful AllStarLink node is the construction of the crossover audio cable.
 - a. Our objective is to make the construction simple for anyone with a wire stripper.
 - b. Cable construction can be a frustration for even the most skilled maker.
 - c. It does not have to be. It no longer is. Solder not required.

2. A little out of the box thinking and using the wide array of available products makes construction straightforward. Tools needed are simple.
 - a. A wire stripper for AWG 26 or smaller wire plus an insulation cutter.
 - b. A small screwdriver usually comes with the connector. That is it.

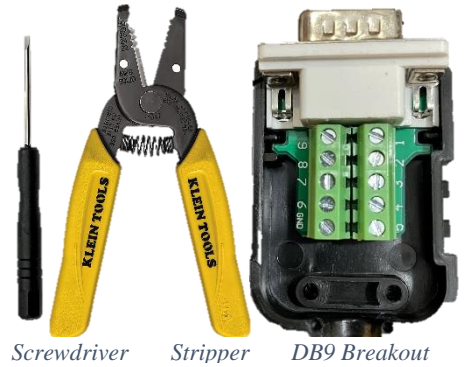3. Parts start with DB9 (D-sub) male non-solder breakout connector. Cost ~ \$7.
 - a. Acquire a pre-manufactured cable having one end that fits the device.
 - b. From the pre-manufactured cable, cut off the unneeded end.
 - c. Strip wires. Tinning (solder coating) is beneficial, but not necessary.
 - d. Place under the terminals of the DB9 and tighten. You are now a maker. Congratulations.



4. Conventional microphones use RJ45 male with an 8Vdc power need. But, the available power from the board is 5V.
 - a. An Alinco EMS-57 mic requires only 5V with a shielded cable & 8-pin round mic connector.



- b. A TYT 7800 is also 5V with a RJ12 modular connector. We still have issues with making its tones work.

DB9	RL 20 Function	Speaker	Alinco	knockoff
1		3.5T red		
2	audio out (Tx) to speak	3.5R wht		
3	COS in from mic PTT		2&7 orange&blk	Blue&yel
4				
5	PTT out			
6	audio in (Rx) from mic		1 yellow	green
7	5VDC solder pad to mic		5 red	red
8	Ground. Bond to gnd lug	3.5S blk	8 grey	black
9				
gn	Gnd lug		8 shield	


5. **Local / Link** digital radio node uses a powered speaker and a mic, 5V DTMF with shield preferred.
 - a. If mic is not Alinco style 8-pin round, acquire an Ethernet extension cable with RJ45 or phone extension with RJ12 female.
 - b. Get an audio repair cable with 3.5mm (1/8") female TRS (tip-ring-sleeve) stereo socket.
 - c. A DB9 solderless connector is the only other item.
 - d. Cut off the opposite end of the Alinco or extension. Look at pin numbers to decipher colors.
 - e. Strip wires, feed through strain relief of DB9. Screw down to pins.
 - f. Alinco pin 7, mic E, connects to cable shield. Jumper to 3. If noisy move to 8.
 - g. Be sure to bond from pin 8-Ground to the gnd lug by pin 6.
 - h. Find an Elmer to solder one thing, a jumper on the board from 5VDC to terminal 7 pad.
 - i. Adjust mic volume: First the screw, then the software according to the Elmer card.



6. **Simplex / Link** node uses a radio which has a COS (carrier-on-switch) signal available.

- a. Baofeng UV are common radios with the capability.
 - b. These radios have a K-head (K-1) connector.
 - c. Acquire an inexpensive Baofeng mic with the proper plugs. Uncoiled is easier. Cost ~ \$8.
 - d. Obtain a 2N7000 FET and a 4.7K resistor to make a COS switch and buffer. Cost ~ \$1.
 - e. A DB9 solderless connector is the next item.
 - f. Remove the cable from the mic. Dispose of the mic.
 - g. Strip wires, feed through strain relief of DB9. Screw down.
 - h. Add the FET – resistor combination under the same DB9 screws with the wires.
 - i. Cover bare wires with heat-shrink or tape to prevent touching.
 - j. The radio duty cycle is 100%. Lower power setting by half to reduce heating.

DB9	RL 20 Function	Radio	FET
1	stereo not used		
2	audio out (Tx) to mic	3.5-r	
3	COS in from FET		Drain - D
4			
5	PTT out	3.5-s	
6	audio in (Rx) from speak	2.5-t	4.7K to gate
7	5VDC solder pad		
8	Ground. Bond to gnd lug	2.5-e	Source - S
9			

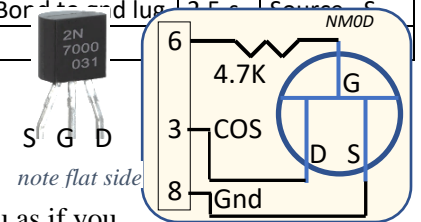

7. If you live where the local repeater is not dependable or you just want to operate on a node someplace else, a simplex or local digital link will connect you as if you are in the same room. Your node is a digital extension of the repeater.



8. Life is good. Enjoy!